



R4 and L1 values can be adjusted for different input/output voltages. Below are a few examples:

| Vin | Vout | R4 | L1 | Iout |
|-----|------|------|-------|------|
| 12V | 230V | 330k | 100µH | 35mA |
| 12V | 300V | 430k | 100µH | 25mA |
| 24V | 230V | 330k | 220µH | 70mA |
| 24V | 300V | 430k | 220µH | 50mA |