

Passive constant-current limiting:

Fig. 7.14 shows some very simple current-limiting arrangements, which could be applied to almost any series stabiliser circuit. Q1 represents the pass device. A **current-sense** resistor R_s is added to the output of the stabiliser to detect the amount of load current being drawn.

In fig. 7.14a., when the load current increases the voltage drop across R_s increases too, until the string of diodes D1-D3 turn on. When this happens current will be ‘stolen’ from the base of the pass device Q1, so restricting the load current to the preset maximum.

If we use ordinary rectifier diodes we may assume a forward drop of about 0.7V each at low current, so the maximum load current, I_{max} , is limited to:

$$I_{max} \approx \frac{N \times 0.7 - V_{be}}{R_s}$$

Where:

N = number of diodes used.

V_{be} = base-emitter voltage of Q1.

Under ideal circumstances once the protection circuit becomes active the output current will not increase beyond the preset maximum; it remains constant even if the output is a dead short circuit. Thus the name ‘constant-current limiting’ is obvious. In practice, it is not quite this perfect, but still good enough for most applications (e.g., see fig. 7.16).

The circuit in fig. 7.14b works in a similar way except that the string of diodes is replaced with a zener diode. In the case of a MOSFET, the zener can also serve to protect against gate-source over-voltage. When the drop across R_s is enough to turn on the zener, current will be diverted through the gate-stopper R_1 , pulling the base voltage of Q1 down, which will in turn reduce the output voltage. The output voltage will fall to whatever voltage is necessary to stop the load current exceeding the preset maximum, which is given by:

$$I_{max} = \frac{V_z - V_{GS}}{R_s}$$

Where:

I_{max} = current limit.

V_z = zener voltage.

V_{GS} = gate-source voltage of Q1 if it is a MOSFET, or V_{be} if it is a BJT.

However, the gate-source voltage of power MOSFETs is highly variable between samples, and increases with drain current, but may be estimated to be in the region of

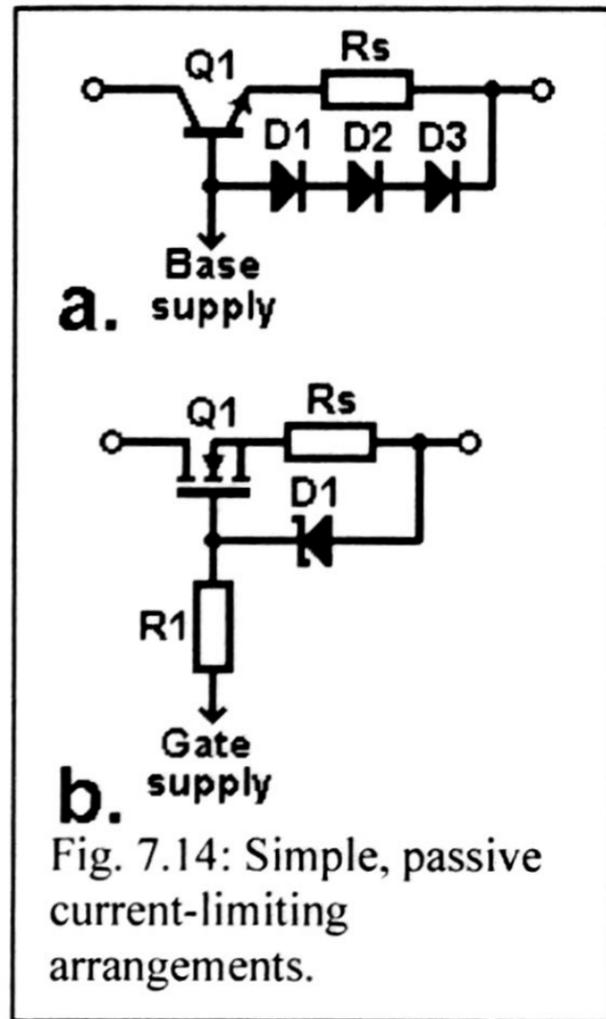


Fig. 7.14: Simple, passive current-limiting arrangements.

4V to 5V for most devices. Also, as seen in the last chapter, diodes do not have a sharply defined turn on characteristic due to their high dynamic resistance at low currents. Thanks to these unpredictable properties, passive current limiting can be rather imprecise. In valve amp applications this does not always matter, however, since we will be usually set I_{max} to a value which is still well below the instantaneous current capability of the devices we are using.

For example, suppose we wished to alter the circuit in fig. 7.11 by limiting its output to 0.5A maximum. We will estimate V_{GS} to be 5V:

$$R_s = \frac{V_z - V_{GS}}{I_{max}} = \frac{12 - 5}{0.5} = 14\Omega.$$

We will use a 10Ω resistor as a convenient standard, which *ought* to limit I_{max} to 0.7A. R_s will dissipate a maximum of $0.7^2 \times 10 = 4.9W$, so a 5W component will do, since such overloads are not expected to be continuous. Additionally, into a short circuit almost all the input voltage must be dropped across the gate-stopper resistor, so it should be at least 1W rated. The circuit is shown in fig. 7.15 and the resulting performance is indicated in fig. 7.16. It can be seen that the actual current limit occurs at about 730mA, and reaches about 740mA into a short circuit; a modest error.

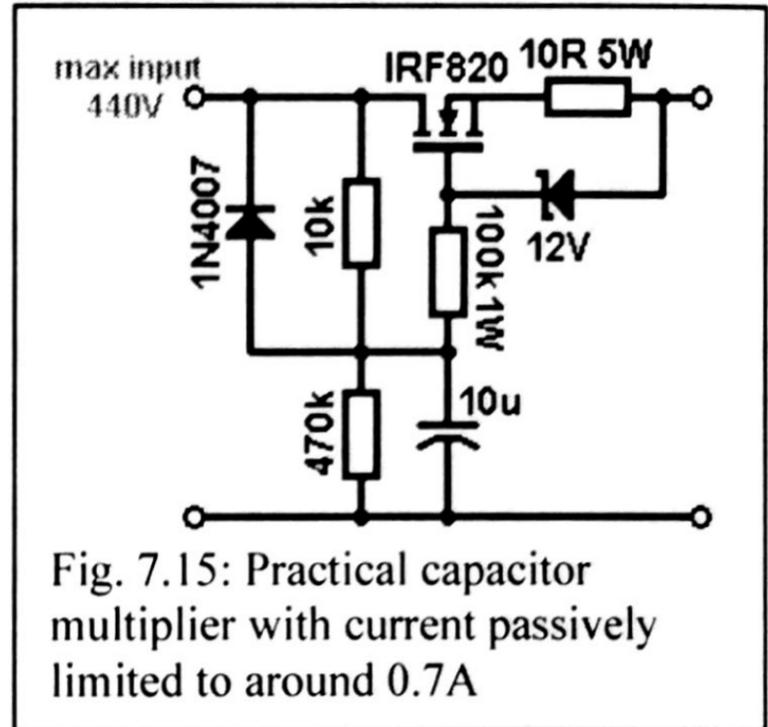


Fig. 7.15: Practical capacitor multiplier with current passively limited to around 0.7A

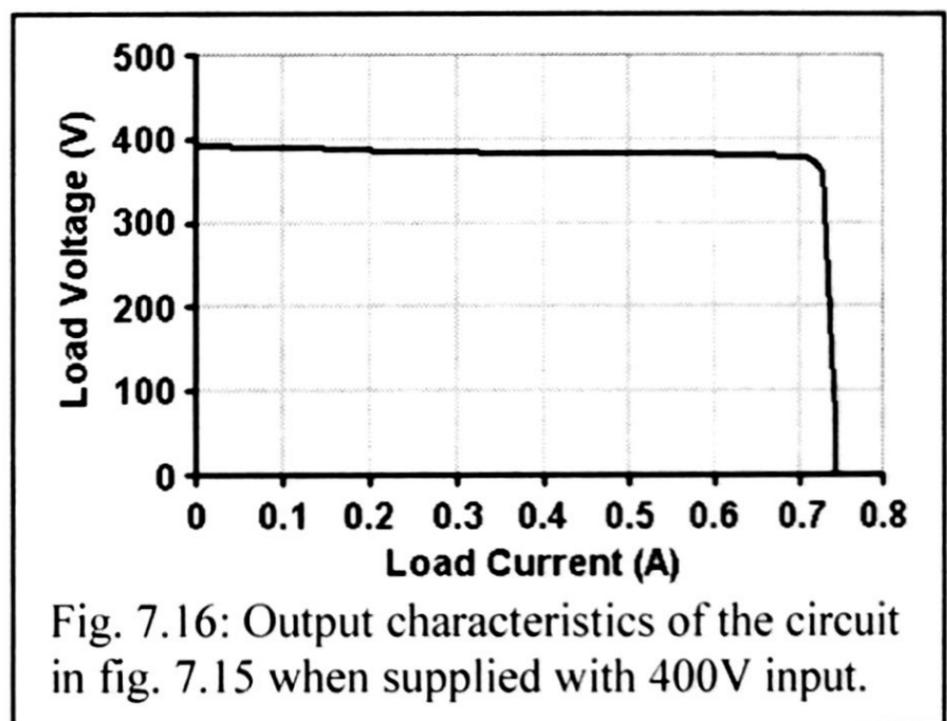


Fig. 7.16: Output characteristics of the circuit in fig. 7.15 when supplied with 400V input.

Active constant-current limiting:

The previous current-limiting techniques are primitive, and the point at which they begin to limit cannot be set precisely without actually testing the components for voltage drop first. Nevertheless, they are still suitable for non-critical circuits. For faster, more accurate current limiting, the circuits in fig. 7.17 are ideal, and are widely used in commercial equipment.

Again, current-sense resistor R_s is added to the output of the stabiliser. Once the voltage drop across this resistor reaches about 0.6V, Q2 will turn on and steal current from the pass device in exactly the same manner as for the circuits discussed previously. With most designs Q2 will have to pass less than a milliamp when on, and since its collector-emitter voltage will be very small, Q2 can be a low voltage, low-power device.